

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specifaction
Implementation
Validation
Tabular
Specification

Predicate Logic and Specifying Circuits

EECS4312: Software Engineering Requirements

JSO, EECS, Lassonde

September 5, 2016

Table of contents

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specifaction
Implementation
Validation
Tabular
Specification

1 Nand Gate

- Functional
- Proof Tree
- Relational

2 Complete & Disjoint Specifications

3 Majority Vote

- Specifaction
- Implementation
- Validation
- Tabular Specification

Nand Gate Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

NAND gate Specification (Complete and Disjoint Function Table)



NAND GATE

Input		Output
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Nand Gate Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification
Implementation
Validation
Tabular
Specification


NAND gate Specification (Complete and Disjoint Function Table)



NAND GATE

Input		Output
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

 Implementation of NAND gate using basic gates



Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} \mid i \leq k \leq j\}$

`nand : THEORY`

`BEGIN`

`BIT: TYPE = subrange(0,1)`

`andf(x:BIT,y:BIT): BIT =`

`COND`

`x=1 AND y=1 -> 1,`

`ELSE -> 0`

`ENDCOND`

`invf(x:BIT): BIT = 1 - x`

Question

Would `BIT: TYPE = {0, 1}` work?

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} | i \leq k \leq j\}$

nand : THEORY

BEGIN

BIT: TYPE = subrange(0,1)

andf(x:BIT,y:BIT): BIT =

COND

x=1 AND y=1 -> 1,

ELSE -> 0

ENDCOND

invf(x:BIT): BIT = 1 - x

Question

Would BIT: TYPE = {0, 1} work?

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} \mid i \leq k \leq j\}$

nand : THEORY

BEGIN

BIT: TYPE = subrange(0,1)

andf(x:BIT,y:BIT): BIT =

COND

x=1 AND y=1 -> 1,

ELSE -> 0

ENDCOND

invf(x:BIT): BIT = 1 - x

Question

Would BIT: TYPE = {0, 1} work?

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} \mid i \leq k \leq j\}$

nand : THEORY

BEGIN

BIT: TYPE = subrange(0,1)

andf(x:BIT,y:BIT): BIT =

COND

x=1 AND y=1 -> 1,

ELSE -> 0

ENDCOND

invf(x:BIT): BIT = 1 - x

Question

Would BIT: TYPE = {0, 1} work?

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} | i \leq k \leq j\}$

nand : THEORY

BEGIN

BIT: TYPE = subrange(0,1)

...

$\text{impf}(x:\text{BIT}, y:\text{BIT}): \text{BIT} =$
 $\text{invf}(\text{andf}(x, y))$

$\text{specf}(x:\text{BIT}, y:\text{BIT}): \text{BIT} =$
COND
 $x = 0 \text{ OR } y = 0 \rightarrow 1,$
 ELSE $\rightarrow 0$
ENDCOND

$\text{verify_functional_implementation}: \text{CONJECTURE}$
 $\text{impf}(x, y) = \text{specf}(x, y)$

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

$\text{subrange}(i,j): \text{TYPE} = \{k : \mathbb{Z} \mid i \leq k \leq j\}$

`nand : THEORY`

`BEGIN`

`BIT: TYPE = subrange(0,1)`

`...`

`impf(x:BIT,y:BIT): BIT =
 invf(andf(x,y))`

`specf(x:BIT, y:BIT): BIT =
 COND
 x = 0 OR y = 0 -> 1,
 ELSE -> 0
 ENDCOND`

`verify_functional_implementation: CONJECTURE
 impf(x,y) = specf(x,y)`

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

`subrange(i,j): TYPE = {k : \mathbb{Z} | $i \leq k \leq j$ }`

`nand : THEORY`

`BEGIN`

`BIT: TYPE = subrange(0,1)`

`...`

`impf(x:BIT,y:BIT): BIT =
 invf(andf(x,y))`

`specf(x:BIT, y:BIT): BIT =
 COND
 x = 0 OR y = 0 -> 1,
 ELSE -> 0
 ENDCOND`

`verify_functional_implementation: CONJECTURE
 impf(x,y) = specf(x,y)`

Nand Gate Specification: Functional

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

subrange(i,j): $\text{TYPE} = \{k : \mathbb{Z} \mid i \leq k \leq j\}$

nand : THEORY

BEGIN


BIT: TYPE = subrange(0,1)

...

impf(x:BIT, y:BIT): BIT =
 invf(andf(x, y))

specf(x:BIT, y:BIT): BIT =
 COND
 x = 0 OR y = 0 -> 1,
 ELSE -> 0
 ENDCOND

 verify_functional_implementation: CONJECTURE
 impf(x, y) = specf(x, y)



Proof Tree

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional


Proof Tree

Relational

Complete &
Disjoint
Specifications

Majority Vote

 Specifaction
Implementation
Validation
Tabular
Specification



Note

M-x x-show-proof brings up a figure like the one on the left.

Question

How do you read the proof tree, starting at the (a) Top or (b) the Bottom? Where are the Axioms? What does the turnstyle represent?

Question

Proof rules transform one sequent into another. How do you interpret the proof rules in the figure?

Proof Tree

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional


Proof Tree

Relational

Complete &
Disjoint
Specifications

Majority Vote

 Specifaction
Implementation
Validation
Tabular
Specification



Note

M-x x-show-proof brings up a figure like the one on the left.

Question

How do you read the proof tree, starting at the (a) Top or (b) the Bottom? Where are the Axioms? What does the turnstyle represent?

Question

Proof rules transform one sequent into another. How do you interpret the proof rules in the figure?

Proof Tree

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional


Proof Tree

Relational

Complete &
Disjoint
Specifications

Majority Vote

 Specifaction
Implementation
Validation
Tabular
Specification



Note

M-x x-show-proof brings up a figure like the one on the left.

Question

How do you read the proof tree, starting at the (a) Top or (b) the Bottom? Where are the Axioms? What does the turnstyle represent?

Question

Proof rules transform one sequent into another. How do you interpret the proof rules in the figure?

Nand Gate Specification: Relational 1

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a,b,c,x,y,z: VAR BIT
```

```
andr(x,y,z): bool =  
  z = (x = 1 AND y = 1)
```

```
invr(x,z): bool =  
  z = (1 - x)
```

```
imp_nandr(a,b,c): bool =  
  (EXISTS (v:BIT) : andr(a,b,v) AND invr(v,c))
```

```
spec_nandr(a,b,c): bool =  
  (c = 0) <=> (a=1 AND b = 1)
```

```
verify_relational_implementation: CONJECTURE  
  imp_nandr(a,b,c) => spec_nandr(a,b,c)
```

Nand Gate Specification: Relational 1

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a,b,c,x,y,z: VAR BIT
```

```
andr(x,y,z): bool =  
  z = (x = 1 AND y = 1)
```

```
invr(x,z): bool =  
  z = (1 - x)
```

```
imp_nandr(a,b,c): bool =  
  (EXISTS (v:BIT) : andr(a,b,v) AND invr(v,c))
```

```
spec_nandr(a,b,c): bool =  
  (c = 0) <=> (a=1 AND b = 1)
```

```
verify_relational_implementation: CONJECTURE  
  imp_nandr(a,b,c) => spec_nandr(a,b,c)
```

Nand Gate Specification: Relational 1

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a,b,c,x,y,z: VAR BIT
```

```
andr(x,y,z): bool =  
    z = (x = 1 AND y = 1)
```

```
invr(x,z): bool =  
    z = (1 - x)
```

```
imp_nandr(a,b,c): bool =  
    (EXISTS (v:BIT) : andr(a,b,v) AND invr(v,c))
```

```
spec_nandr(a,b,c): bool =  
    (c = 0) <=> (a=1 AND b = 1)
```

```
verify_relational_implementation: CONJECTURE  
    imp_nandr(a,b,c) => spec_nandr(a,b,c)
```

Nand Gate Specification: Relational 1

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification
Implementation
Validation
Tabular
Specification

```
a, b, c, x, y, z: VAR BIT
```

```
andr(x, y, z): bool =  
    z = (x = 1 AND y = 1)
```

```
invr(x, z): bool =  
    z = (1 - x)
```

```
imp_nandr(a, b, c): bool =  
    (EXISTS (v:BIT) : andr(a, b, v) AND invr(v, c))
```

```
spec_nandr(a, b, c): bool =  
    (c = 0) <=> (a=1 AND b = 1)
```

```
verify_relational_implementation: CONJECTURE  
    imp_nandr(a, b, c) => spec_nandr(a, b, c)
```

Nand Gate Specification: Relational 1

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification
Implementation
Validation
Tabular
Specification

```
a, b, c, x, y, z: VAR BIT
```

```
andr(x, y, z): bool =  
    z = (x = 1 AND y = 1)
```

```
invr(x, z): bool =  
    z = (1 - x)
```

```
imp_nandr(a, b, c): bool =  
    (EXISTS (v:BIT) : andr(a, b, v) AND invr(v, c))
```

```
spec_nandr(a, b, c): bool =  
    (c = 0) <=> (a=1 AND b = 1)
```

```
verify_relational_implementation: CONJECTURE  
    imp_nandr(a, b, c) => spec_nandr(a, b, c)
```

Nand Gate Specification: Relational 2

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a, b, c, x, y, z: VAR BIT
```

```
andr(x, y, z): bool =  
  z = (x = 1 AND y = 1)
```

```
invr(x, z): bool =  
  z = (1 - x)
```

```
imp_nandr(a, b, c): bool =  
  (EXISTS (v:BIT) : andr(a, b, v) AND invr(v, c))
```

Note

The dummy variable v allows us to wire the output of the AND gate to the input of the INVERTER.

The Existential Quantifier allows us to hide the dummy variable. Thus the only free variables of `imp_nandr` are the inputs a and b and the output c .

Nand Gate Specification: Relational 2

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a, b, c, x, y, z: VAR BIT
```

```
andr(x, y, z): bool =  
  z = (x = 1 AND y = 1)
```

```
invr(x, z): bool =  
  z = (1 - x)
```

```
imp_nandr(a, b, c): bool =  
  (EXISTS (v:BIT) : andr(a, b, v) AND invr(v, c))
```

Note

The dummy variable v allows us to wire the output of the AND gate to the input of the INVERTER.

The Existential Quantifier allows us to hide the dummy variable. Thus the only free variables of `imp_nandr` are the inputs a and b and the output c .

Nand Gate Specification: Relational 2

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
a, b, c, x, y, z: VAR BIT
```

```
andr(x, y, z): bool =  
  z = (x = 1 AND y = 1)
```

```
invr(x, z): bool =  
  z = (1 - x)
```

```
imp_nandr(a, b, c): bool =  
  (EXISTS (v:BIT) : andr(a, b, v) AND invr(v, c))
```

Note

The dummy variable v allows us to wire the output of the AND gate to the input of the INVERTER.

The Existential Quantifier allows us to hide the dummy variable. Thus the only free variables of `imp_nandr` are the inputs a and b and the output c .

Complete and Disjoint Specifications

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

NAND gate Specification
(Complete and Disjoint
Function Table)



NAND GATE

Input		Output
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Question 1

What does it mean for a function table to be (a) Complete and (b) Disjoint?

Question 2

What is the significance of (a) Completeness and (b) Disjointness?

Complete and Disjoint Specifications

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification
Implementation
Validation
Tabular
Specification

NAND gate Specification
(Complete and Disjoint
Function Table)



NAND GATE

Input		Output
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Question 1

What does it mean for a function table to be (a) Complete and (b) Disjoint?

Question 2

What is the significance of (a) Completeness and (b) Disjointness?

Complete and Disjoint Specifications

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

NAND gate Specification
(Complete and Disjoint
Function Table)



NAND GATE

Input		Output
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Question 1

What does it mean for a function table to be (a) Complete and (b) Disjoint?

Question 2

What is the significance of (a) Completeness and (b) Disjointness?

Majority Voting Circuit Specification


Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

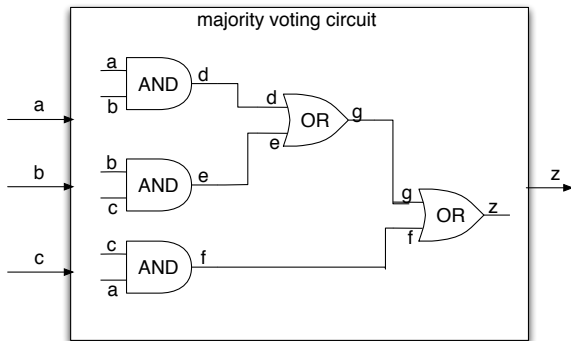Majority Vote
Specification
Implementation
Validation
Tabular
Specification



Question

What is a complete and disjoint function table for the majority Voting Circuit?

Majority Voting Circuit Specification


Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

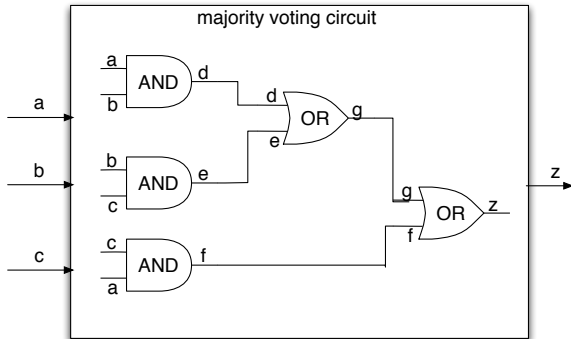Majority Vote
Specification
Implementation
Validation
Tabular
Specification



Question

What is a complete and disjoint function table for the majority Voting Circuit?

Majority Voting Circuit Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification

Implementation
Validation

Tabular
Specification

majority_vote: **THEORY**

BEGIN

BIT: **TYPE** = subrange(0,1) CONTAINING 0
 % what would happen without "containing 0"?

a,b,c,z : BIT *% input and output*

% Majority Vote Specification

spec: **bool** =

$z = 1 \iff (a + b + c \geq 2)$

Majority Voting Circuit Implementation

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote

Specification
Implementation
Validation
Tabular
Specification

```
andGate(v,w,x: BIT): bool =           % define and_gate
    x=1 IFF (v=1 AND w=1)
```

```
orGate(v,w,x:BIT): bool =             % define or_gate
    x=1 IFF (v=1 OR w=1)
```

```
implementation: bool =                % implementation
    (exists (d,e,f,g: BIT):
        andGate(a,b,d)
        AND andGate(b,c,e)
        AND andGate(c,a,f)
        AND orGate(d,e,g)
        AND orGate(g,f,z)
    )
```

Validation

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate
Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

```
implementation_correctness: CONJECTURE  
  implementation  
  IMPLIES  
  spec
```

% Check that antecedent of above is not false. Why?

```
implementable: CONJECTURE  
  a=1 AND b=1 AND c=1 AND z=1  
  IMPLIES  
  implementation /= False
```

```
END majority_vote
```


Tabular Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
**Tabular
Specification**

Complete and Disjoint Table

What is completeness? What is Disjointness?

Input	z
$a + b + c \geq 2$	1
$a + b + c < 2$	0

Assume $a, b, c \in \{0, 1\}$

Tabular Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

Complete and Disjoint Table

What is completeness? What is Disjointness?

Input	z
$a + b + c \geq 2$	1
$a + b + c < 2$	0

Assume $a, b, c \in \{0, 1\}$

Tabular Specification

Circuits

EECS4312:
Software
Engineering
Requirements

Nand Gate

Functional
Proof Tree
Relational

Complete &
Disjoint
Specifications

Majority Vote
Specification
Implementation
Validation
Tabular
Specification

Complete and Disjoint Table

What is completeness? What is Disjointness?

Input	z
$a + b + c \geq 2$	1
$a + b + c < 2$	0

Assume $a, b, c \in \{0, 1\}$