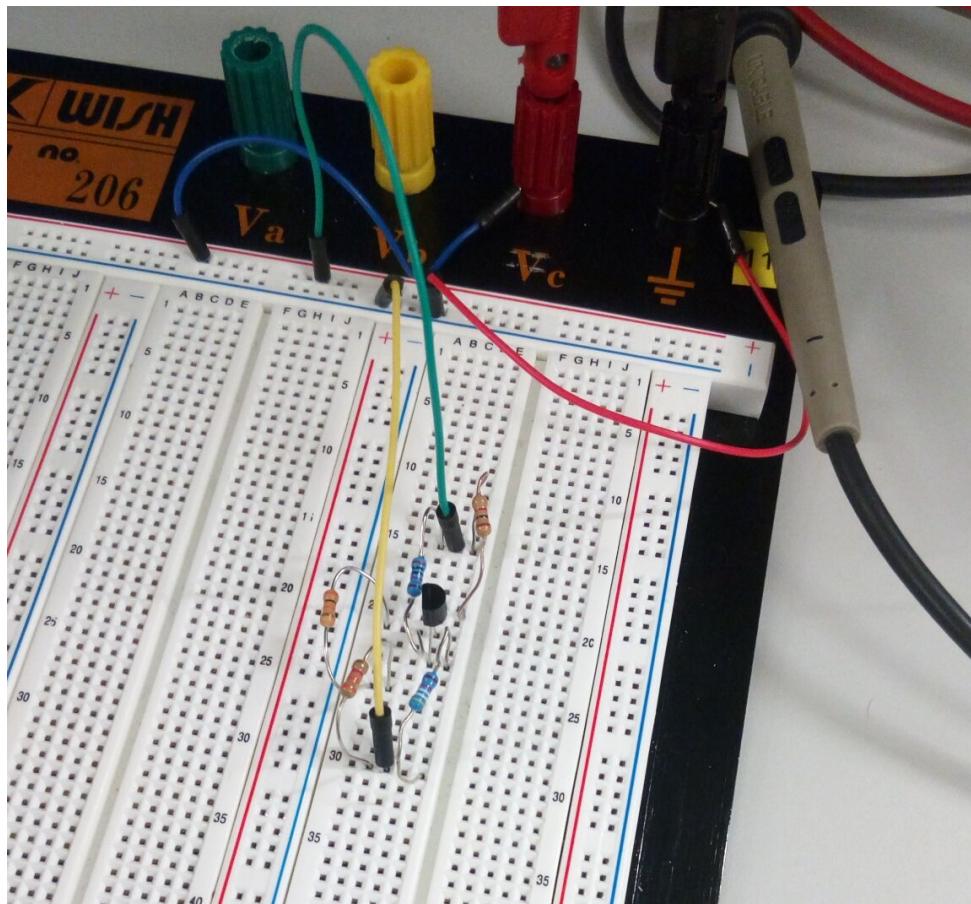


1. We tested the transistor with a multi-meter and found it to be working.
2. We assembled the circuit like so



3. We measured  $i_c$  to be 0.23mA and  $V_{ce}$  to be 0.0016V
4. We did the calculations to determine which resistors to use

$$15 \cdot \frac{R_2}{R_1 + R_2} = 3.1V$$

$$R_2 = 0.25R_1 + 0.25R_2$$

$$R_2 = 0.23R_1$$

$$\frac{R_1}{R_2} = 3$$

We used a 30k and 10k resistors.

5.  $P = V_{ce} \cdot I_c$

$$= 6V \cdot 3mA = 18mW$$

#### Analysis

The pre-lab values implied that the transistor was in saturation instead of active, this was found to be true in the lab. In this lab we learned how the resistors influence the  $I_c$  of a bjt, and we learned this through much trial and error. It took us a long time to find a working combination of resistors, but after we found them we learned a lot about the operation of bjts.